
EE560: Power Electronics Converters

Name - SATYAM MISHRA

Roll No - 224102108

GRID FOLLOWING CONVERTER

1 Objective:

Simulate closed loop control of three-phase four-wire grid following converter using current control loop in dq0 frame. The total dc link voltage is maintained at 1000 V. Assume line of impedance $R = 0.1 \Omega$, $L = 0.01 \text{ mH}$ and grid voltage is 400 V at 50 Hz. The converter is connected to grid through an LC filter. Choose appropriate value of L and C of filter. Show the performance during following cases (a) Supplying $P = 5 \text{ kW}$, $Q = 2 \text{ kVAr}$ to grid. (b) Absorbing $P = 5 \text{ kW}$, $Q = 2 \text{ kVAr}$ from grid.

2 Design of Grid Following Converter Design:

2.1 Calculation of LC filter

- $\omega_o = \frac{1}{\sqrt{LC}}$
- here $\omega_o = 314 \text{ rad/sec}$ Assume $L = 100 \text{ mH}$
- $C = 20.26 \mu \text{ F}$

2.2 Procedure

In Grid Following we usually use current control method

1. First we generate reference current I_d^*, I_q^* using series RLC load which is getting real power $P = 5 \text{ kW}$, reactive power $Q = 2 \text{ kVAr}$ getting power from three phase source
2. Comparing the output current with reference current passing from PI controller to minimize the error, then give this to PWM block thus we generate pwm pluses and given them to switches.
3. After sending the PWM signal into 2 level inverter, connecting to load real power $P = 5 \text{ kW}$, reactive power $Q = 2 \text{ kVAr}$ with by a LC filter.
4. For case 2 we change the value pf P and Q, $P = -5 \text{ kW}$, reactive power $Q = -2 \text{ kVA}$.

3 MATLAB simulation Grid Following Converter :

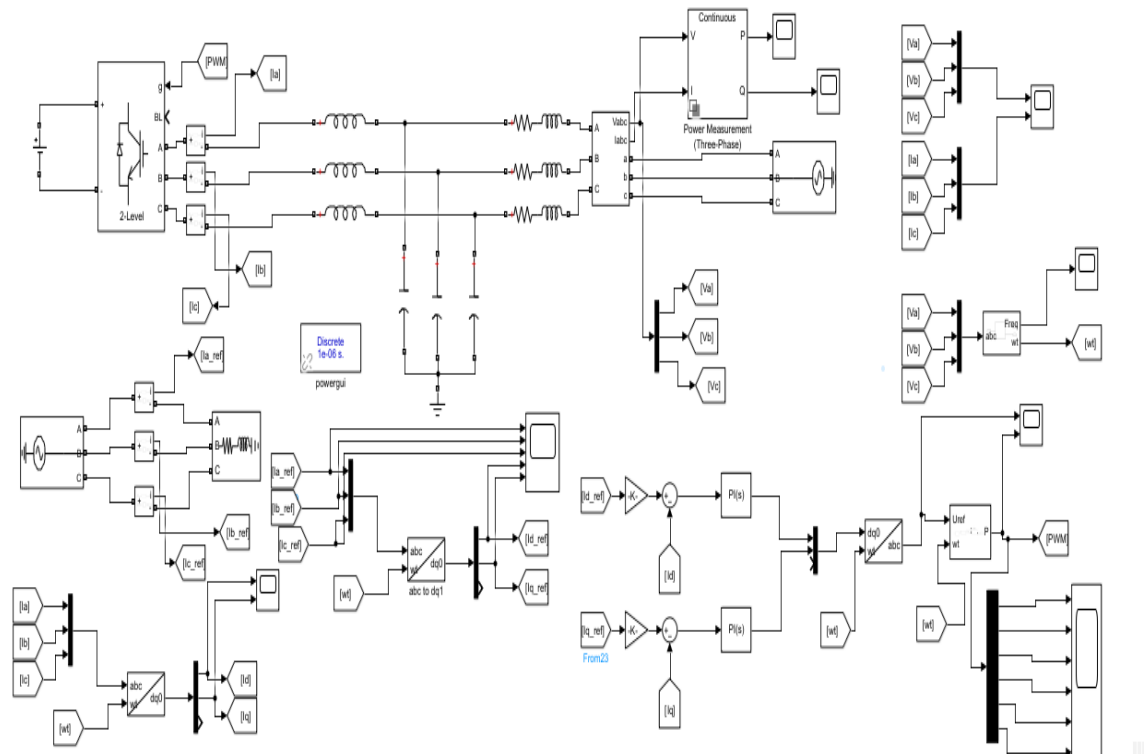


Fig. 1: Simulated Diagram of Grid Following Converter

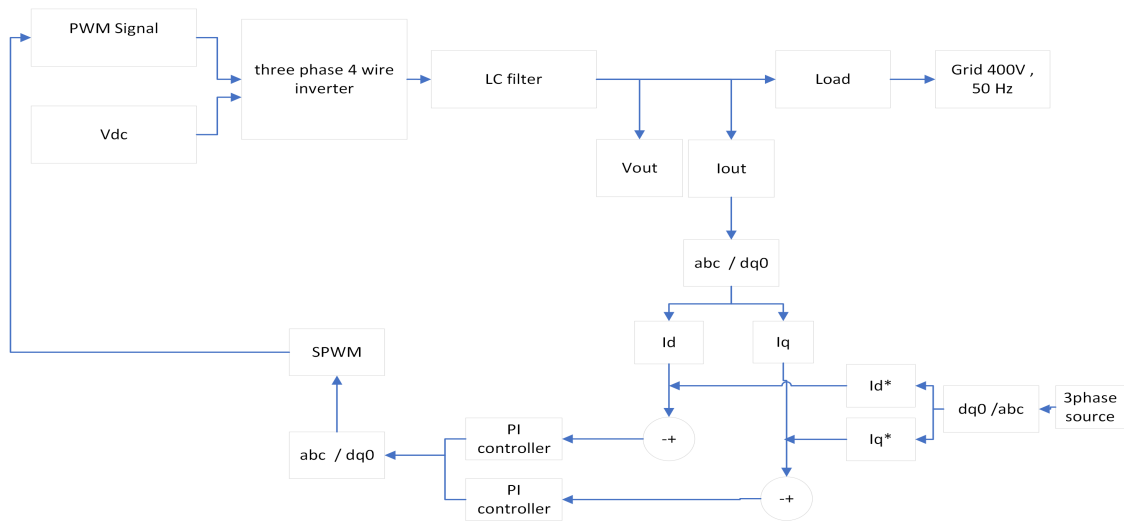


Fig. 2: Block Diagram of Grid Following Converter

3.1 waveform

3.2 Case 1 : Supplying $P = 5 \text{ kW}$, $Q = 2 \text{ kVAr}$ to grid.

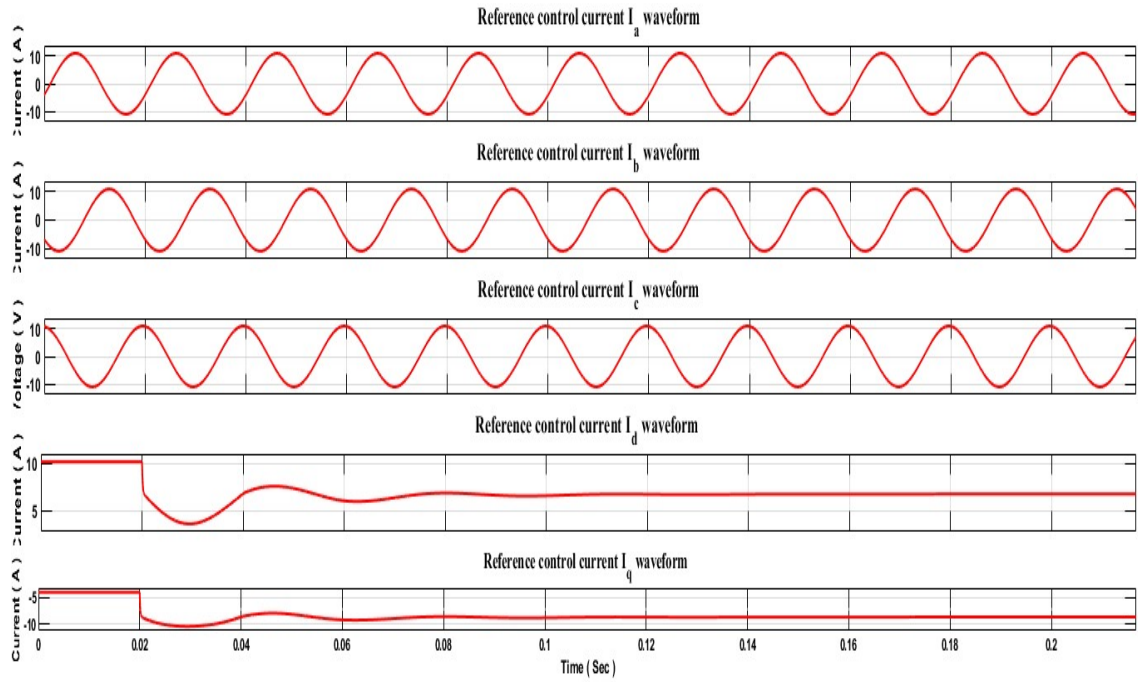


Fig. 3: Reference Control Voltage waveform

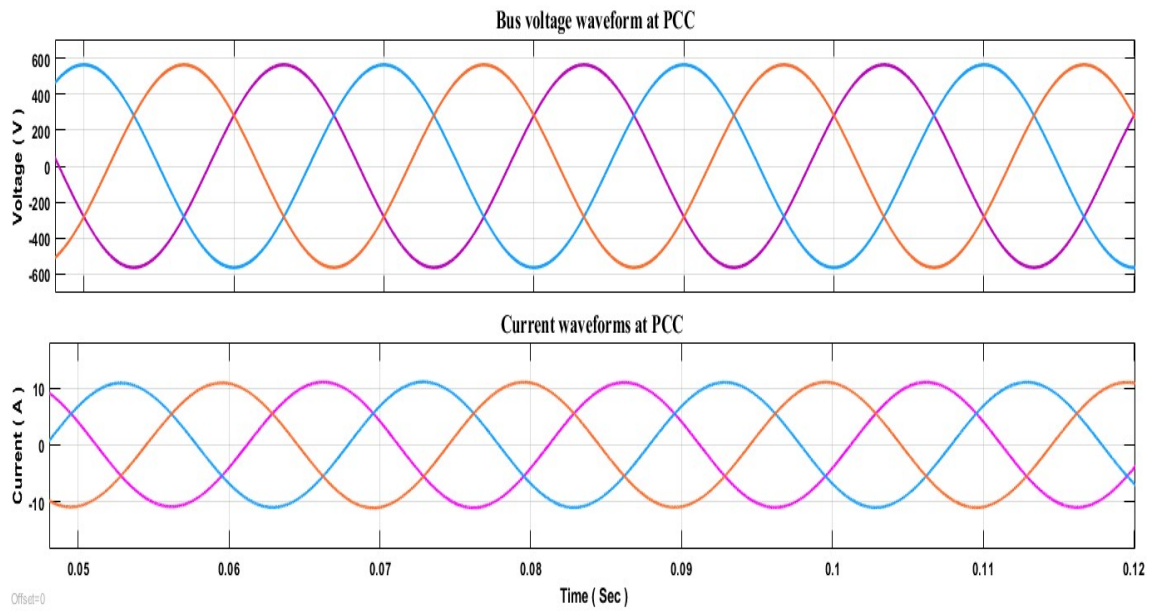


Fig. 4: Bus voltage and bus current waveform at PCC

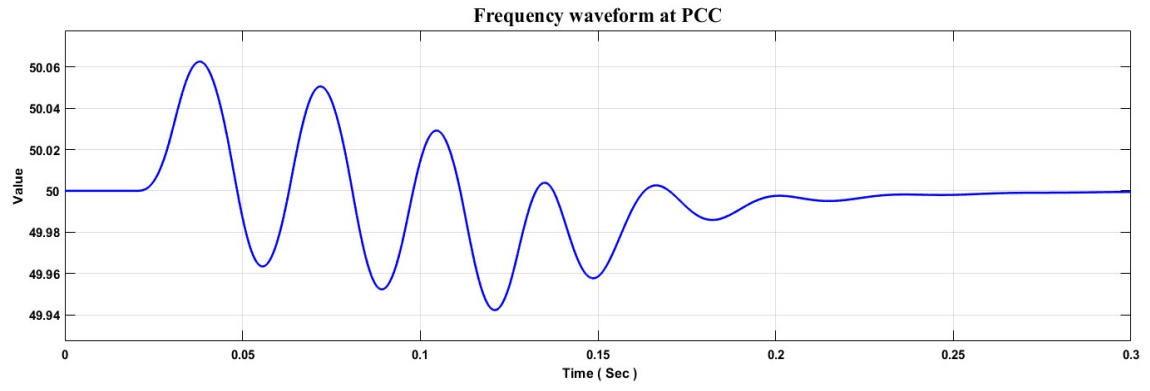


Fig. 5: Frequency at PCC

3.3 Observation

Parameter	Value
Active Power at PCC	4.98 kW
Reactive power at PCC	3.27 kVAr

Table 1: Active and Reactive power at PCC

3.4 Case 2 : Absorbing $P = \text{kW}$, $Q = 2 \text{ kVAr}$ from grid

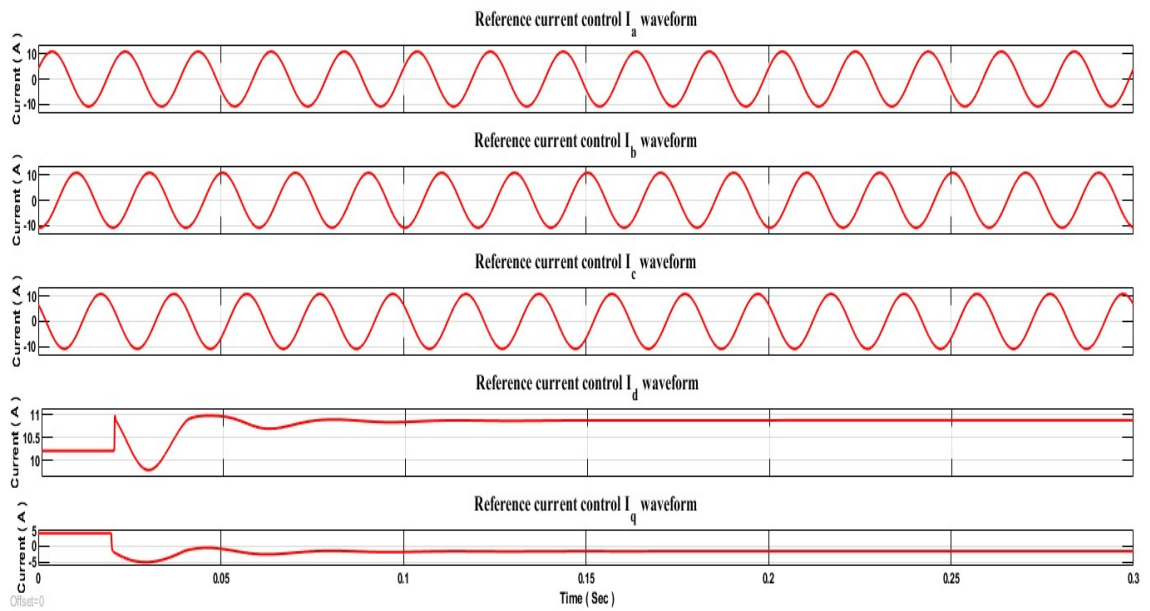


Fig. 6: Reference Control Voltage

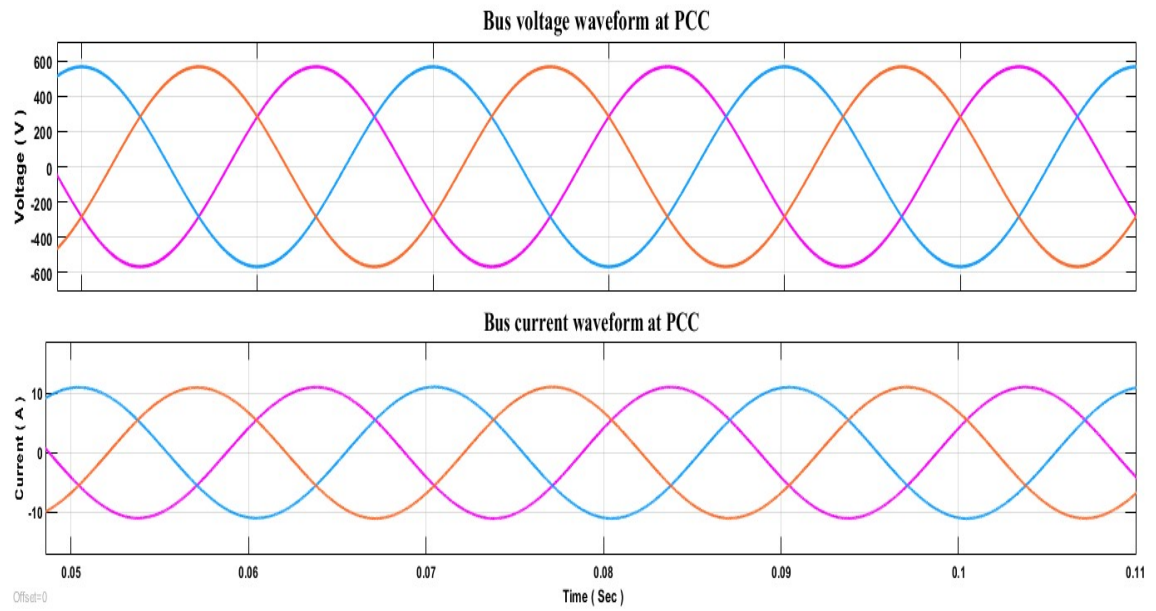


Fig. 7: Bus Voltage and bus Current at PCC

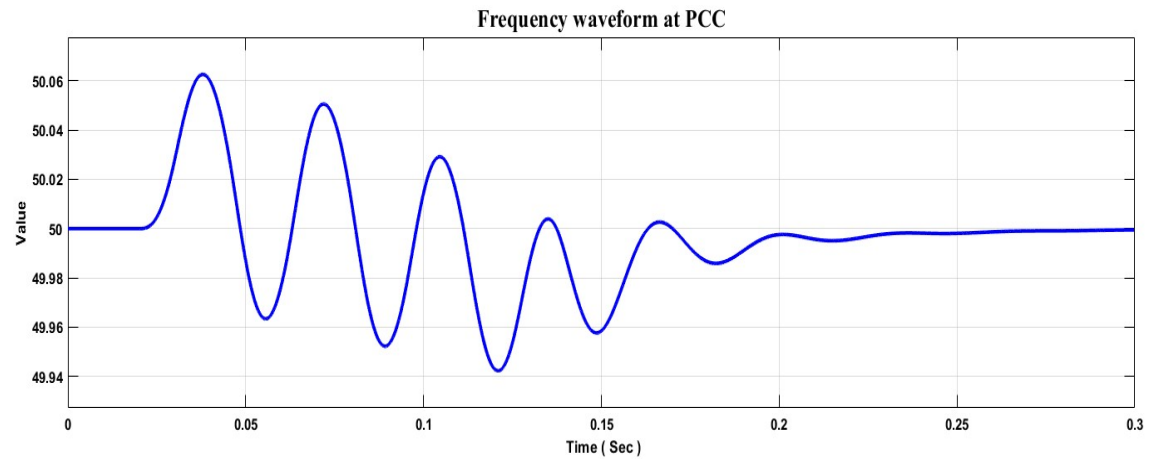


Fig. 8: Frequency at PCC

3.5 Observation

Parameter	Value
Active Power at PCC	- 5.12 kW
Reactive power at PCC	- 2.56 kVAr

Tabel 2: Active and Reactive power at PCC

GRID FORMING CONVERTER

1 Objective:

Simulate closed loop control of three-phase four-wire grid forming converter using current control loop in dq0 frame. The total dc link voltage is maintained at 1000 V. Grid voltage is 400 V at 50 Hz. The converter is connected to load through an LC filter. Choose appropriate value of L and C of filter. Show the performance when load changes from 10 kW to 12 kW.

2 Design of Grid Forming Converter Design:

2.1 Calculation of LC filter

- $\omega_o = \frac{1}{\sqrt{LC}}$
- here $\omega_o = 314$ rad/sec Assume L= 100 mH
- C = 20.26 μ F

2.2 Procedure

In Grid Forming we usually use current control method

1. First we generate reference voltage V_{d^*}, V_{q^*} using three phase source
2. Comparing the output voltage with reference voltage passing from PI controller in order to minimize the error , then give this to PWM block thus we generate pwm pulses and given them to switches.
3. After sending the PWM signal into 2 level inverter, connecting with load by a LC filter .

3 MATLAB simulation Grid Forming Converter :

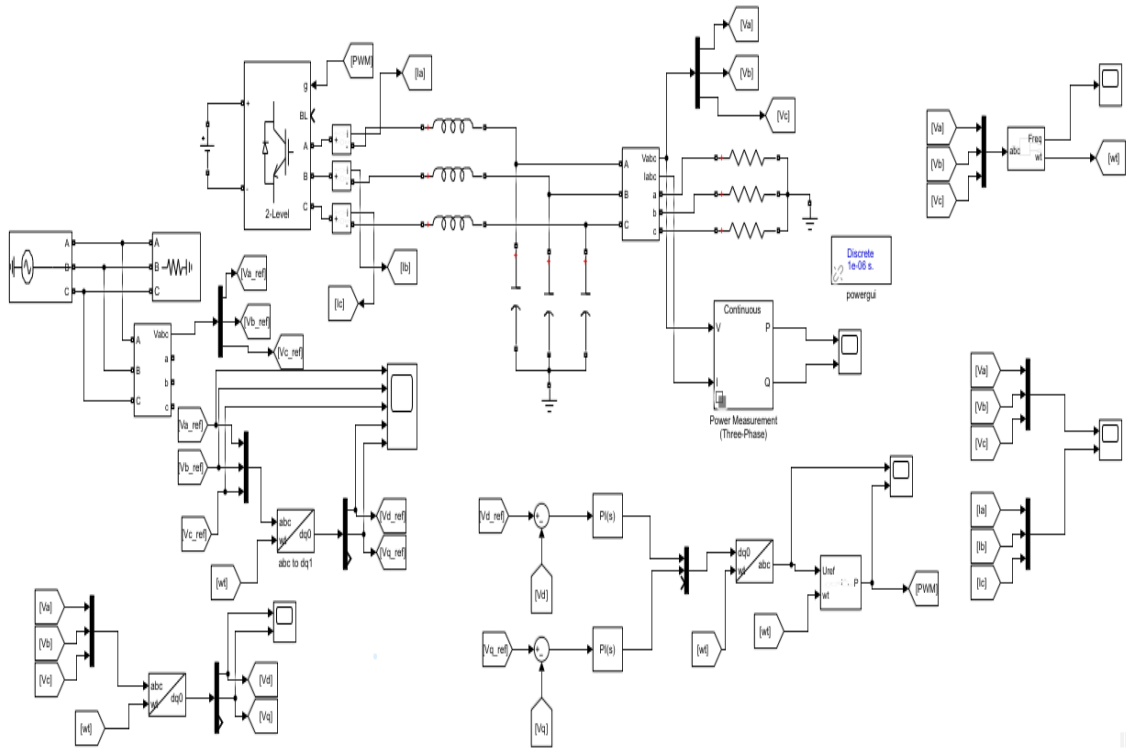


Fig. 1: Simulated Diagram of Grid Forming Converter

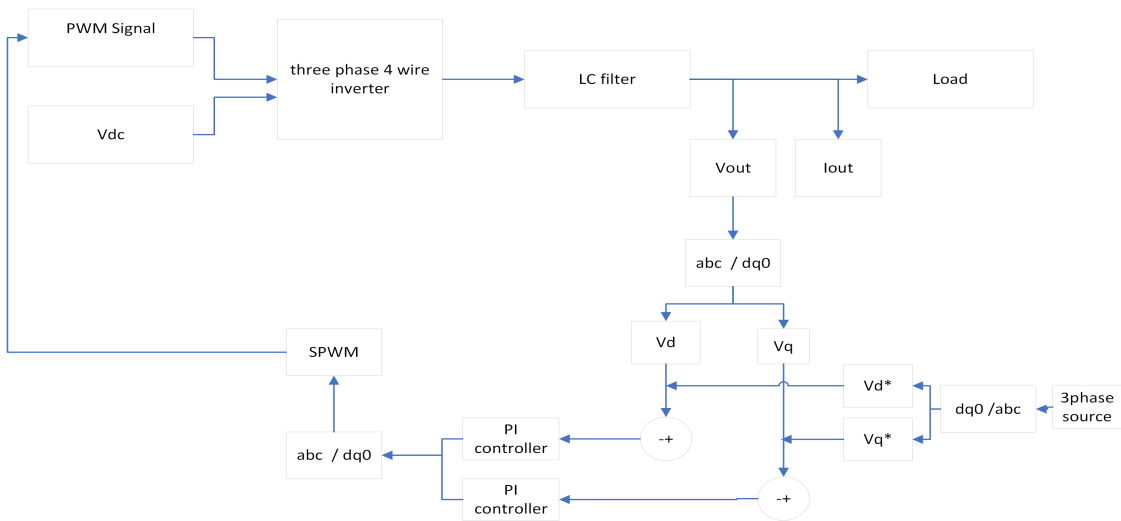


Fig. 2: Block Diagram of Grid Forming Converter

3.1 waveform

3.2 Case 1 : When Load = 10 kW

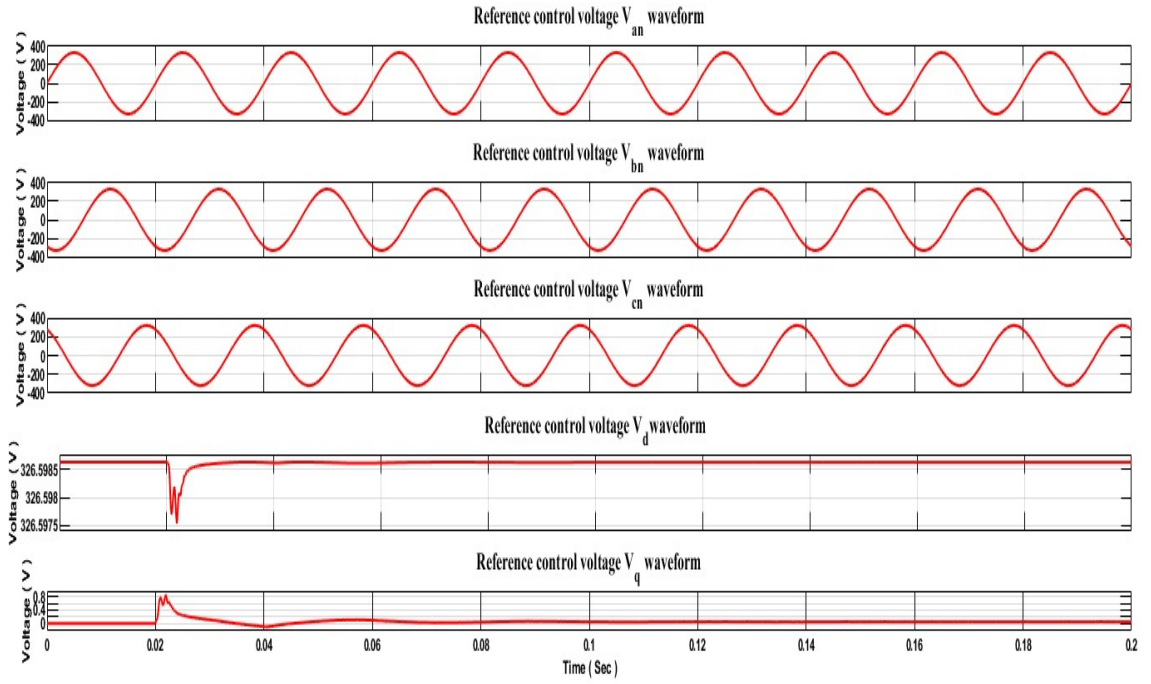


Fig. 3: Reference Control Voltage waveform

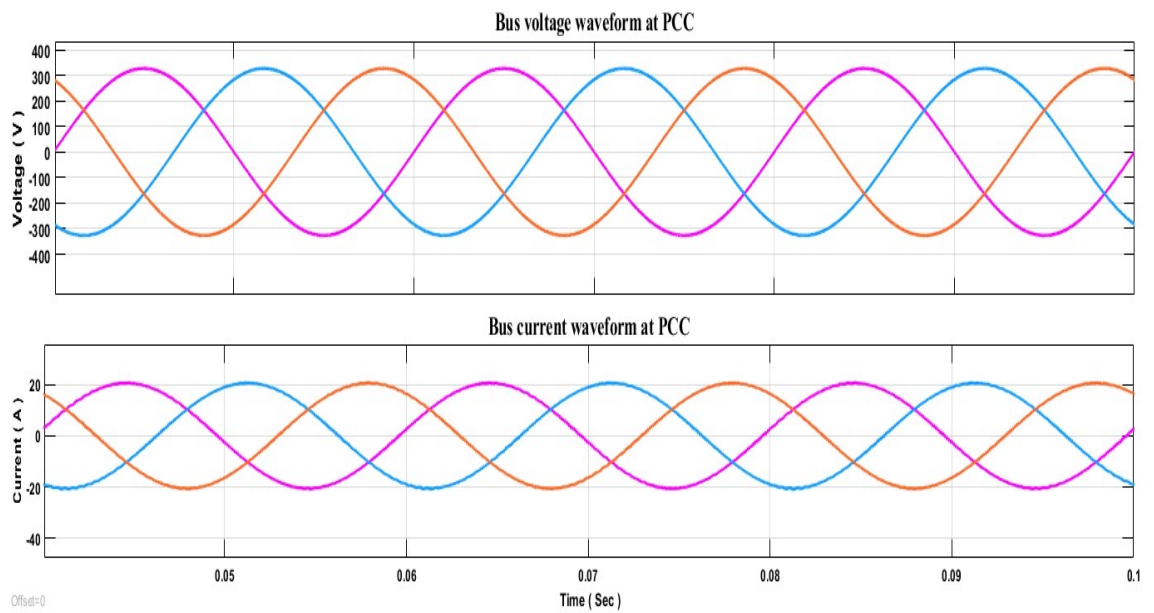


Fig. 4: Bus voltage and bus current waveform at PCC

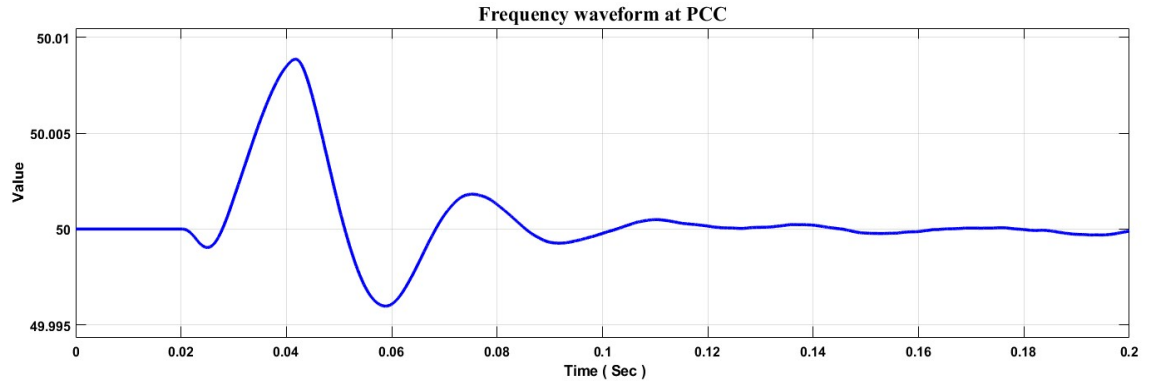


Fig. 5: Frequency at PCC

3.3 Observation

Parameter	Value
Active Power at PCC	9.96 kW
Reactive power at PCC	0 kVAr

Tabel 1: Active and Reactive power at PCC

3.4 Case 2 : When Load = 12 kW

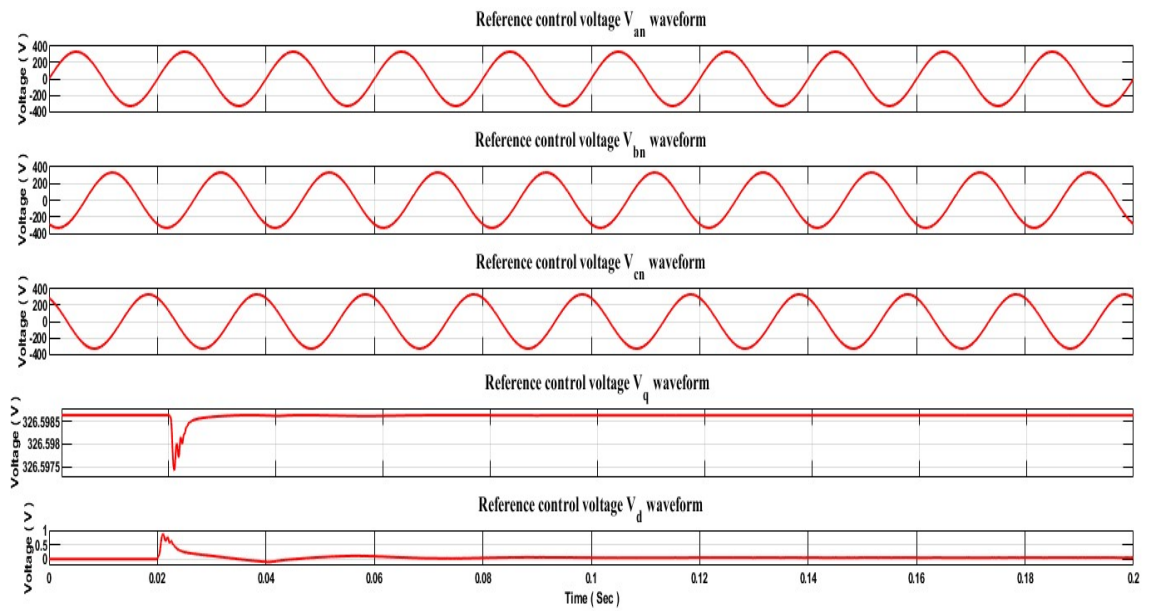


Fig. 6: Reference Control Voltage

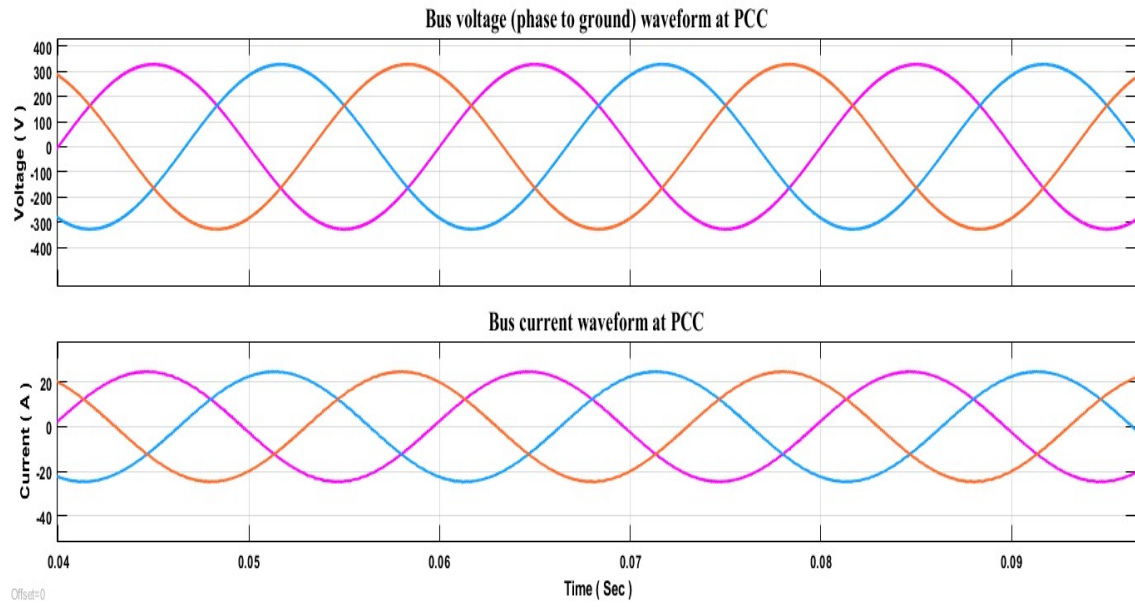


Fig. 7: Bus Voltage and bus Current at PCC

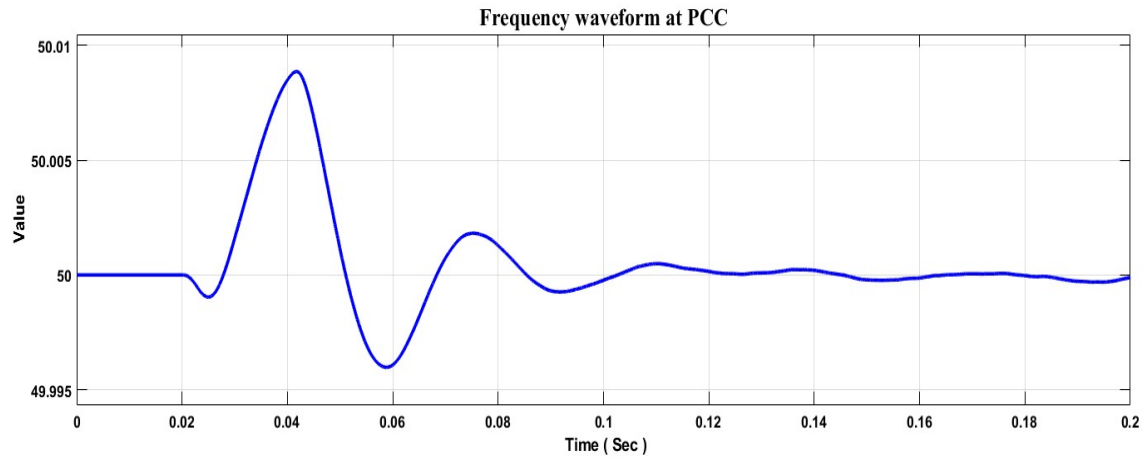


Fig. 8: Frequency at PCC

3.5 Observation

Parameter	Value
Active Power at PCC	11.64 kW
Reactive power at PCC	0 kVAr

Tabel 2: Active and Reactive power at PCC